

# UNIVERSITY OF MIAMI

Department of Electrical and Computer Engineering  
ECE 203

Name: \_\_\_\_\_  
Section: \_\_\_\_\_  
Date: \_\_\_\_\_

## EXPERIMENT 1

### VOLTAGE DIVISION

**PURPOSE:** The purpose of this lab is to introduce a new student to the basics of electric measurements through the use of a simple voltage divider circuit.

#### *Equipment*

---

- 1 Variable resistance box
- 1 Digital voltmeter (DVM)
- 1 D.C. power supply
- 1 Function generator
- 1 Oscilloscope

#### *Preliminary Work*

---


Fig. 1.1 shows a voltage divider circuit. For this circuit find:

- a) The current  $I$  in terms of  $V_s$ ,  $R_1$ , and  $R_L$ ;
- b) The voltage across  $R_L$ ;
- c) The DC power delivered to  $R_L$ , and
- d) The power supplied by the source.
- e) Request the instructor's help to gather information in order to answer discussion item (d).

## Experimental Procedure

### I. D.C. Measurements:

- a) Set up the circuit shown in Fig. 1.1. Measure and record the actual value of  $R_1$ .

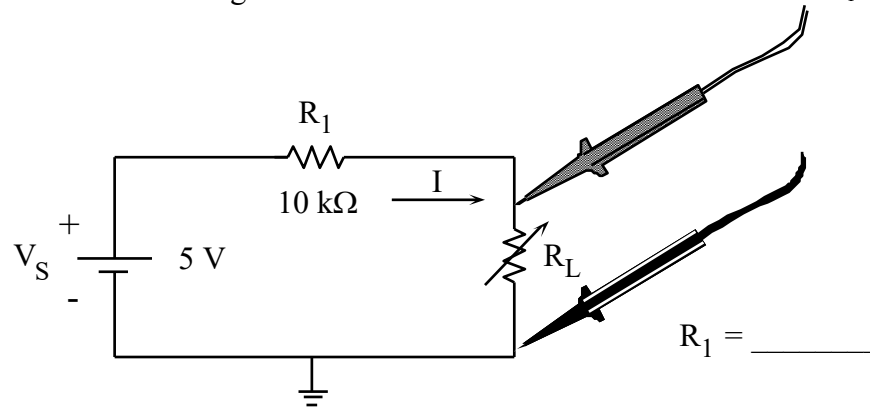

**Figure 1.1** Simple voltage divider circuit with DVM probes shown.

- b) Set the dc power supply to 5 V. Measure the voltages across  $R_1$  and  $R_L$  using the DVM as shown in Fig. 1.1 (Set the DVM to measure DC). Vary the  $R_L$  to the values given in Table 1.1; measure the voltages at each point. Enter all the values in the table under the column labeled “MEASURED”.
- c) Calculate the voltages across the resistors  $R_1$  and  $R_L$  for all values of  $R_L$  shown in Table 1.1 using the formulas from your preliminary work. Enter the voltages in the table under the column labeled “CALCULATED”. Compare  $V_{RL}$  against the measured value by calculating the percentage error. Remember that the percentage error can be found from

$$\% \text{ Error} = \left| \frac{\text{Calculated value} - \text{Measured value}}{\text{Calculated value}} \right| \times 100\%.$$


Show a set of calculations for  $V_{R1}$ ,  $V_{R2}$ , and %Error on  $V_{RL}$  in detail.

$R_L$ (KΩ)	Measured		Calculated		
	$V_{R1}$ (V)	$V_{RL}$ (V)	$V_{R1}$ (V)	$V_{RL}$ (V)	% Error ( $V_{RL}$ )
1					
5					
10					
15					
20					
40					

Measured value of  $V_s$  = \_\_\_\_\_ V

**Table 1.1** Measured and calculated dc voltages using DVM

- d) Repeat parts (a) - (c) but use the oscilloscope instead of the DVM (see Fig. 1.2). Record your values in Table 1.2. Measure and record the actual value of  $R_1$ . Note that the measurement has to be taken as  $V_{R1}=V_S-V_{RL}$ .

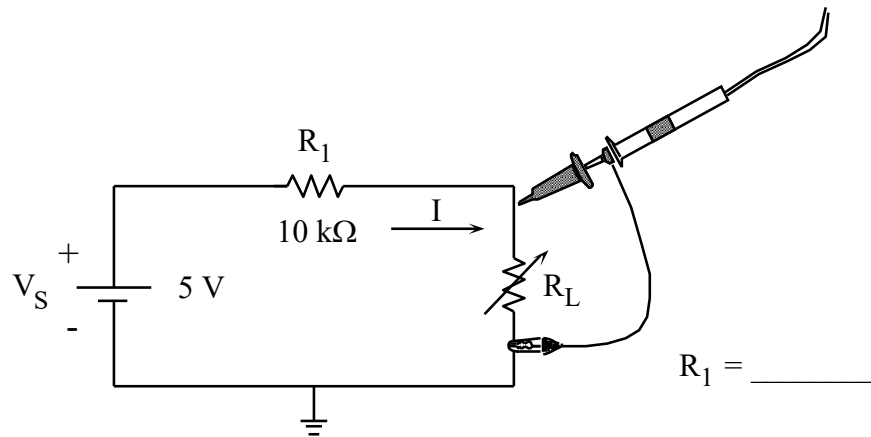

**Figure 1.2** Simple voltage divider circuit with oscilloscope probes shown.

<b><math>R_L</math> (K<math>\Omega</math>)</b>	<b>Measured</b>		<b>Calculated</b>		
	<b><math>V_{R1}</math> (V)</b>	<b><math>V_{RL}</math> (V)</b>	<b><math>V_{R1}</math> (V)</b>	<b><math>V_{RL}</math> (V)</b>	<b>% Error (<math>V_{RL}</math>)</b>
1					
5					
10					
15					
20					
40					

Measured value of  $V_s$  = \_\_\_\_\_ V

**Table 1.2** Measured and calculated dc voltages using oscilloscope.

## II. AC Measurements:

- a) *DVM measurements:* Replace the dc power supply in Fig. 1.1 with the frequency (function) generator. Adjust the voltage to 5 V<sub>p-p</sub> at 1 kHz. Repeat parts (a) - (c) of the dc measurements. Tabulate your data in Table 1.3. Note that the DVM should be in AC mode in order to measure AC rms. values.

<b>R<sub>L</sub> (K<math>\Omega</math>)</b>	<b>Measured</b>		<b>Calculated</b>		
	<b>V<sub>R1</sub> (V)</b>	<b>V<sub>RL</sub> (V)</b>	<b>V<sub>R1</sub> (V)</b>	<b>V<sub>RL</sub> (V)</b>	<b>% Error (V<sub>RL</sub>)</b>
1					
5					
10					
15					
20					
40					

Measured value of  $V_s = \underline{\hspace{2cm}} V_{\text{rms}}$

**Table 1.3** Measured and calculated rms. AC voltages using DVM.

- b) *Oscilloscope measurements:* Repeat part (a) of the ac measurements using the oscilloscope. Tabulate your data in Table 1.4.

<b>R<sub>L</sub> (K<math>\Omega</math>)</b>	<b>Measured</b>		<b>Calculated</b>		
	<b>V<sub>R1</sub> (V)</b>	<b>V<sub>RL</sub> (V)</b>	<b>V<sub>R1</sub> (V)</b>	<b>V<sub>RL</sub> (V)</b>	<b>% Error (V<sub>RL</sub>)</b>
1					
5					
10					
15					
20					
40					


Measured value of  $V_s = \underline{\hspace{2cm}} V_{\text{p-p}}$

**Table 1.4** Measured and calculated peak-to-peak AC voltages using oscilloscope.

## ***Discussion of Results***

---

- a) Comment on the benefits of using either the DVM or the SCOPE for particular situations.
- b) Find the current in the circuit of Fig. 1.1 when  $R_L = 50 \text{ k}\Omega$ .
- c) In the circuit of Fig. 1.3  $R_1$  is fixed. Derive the condition under which maximum power will be delivered to  $R_2$ . Why?

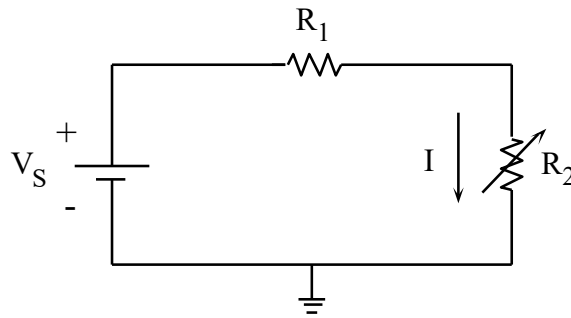

**Figure 1.3** Simple voltage divider circuit.

- d) Prepare a table indicating the possible measurements that can be carried out using each equipment you used during the experiment.
- e) Write a conclusion.